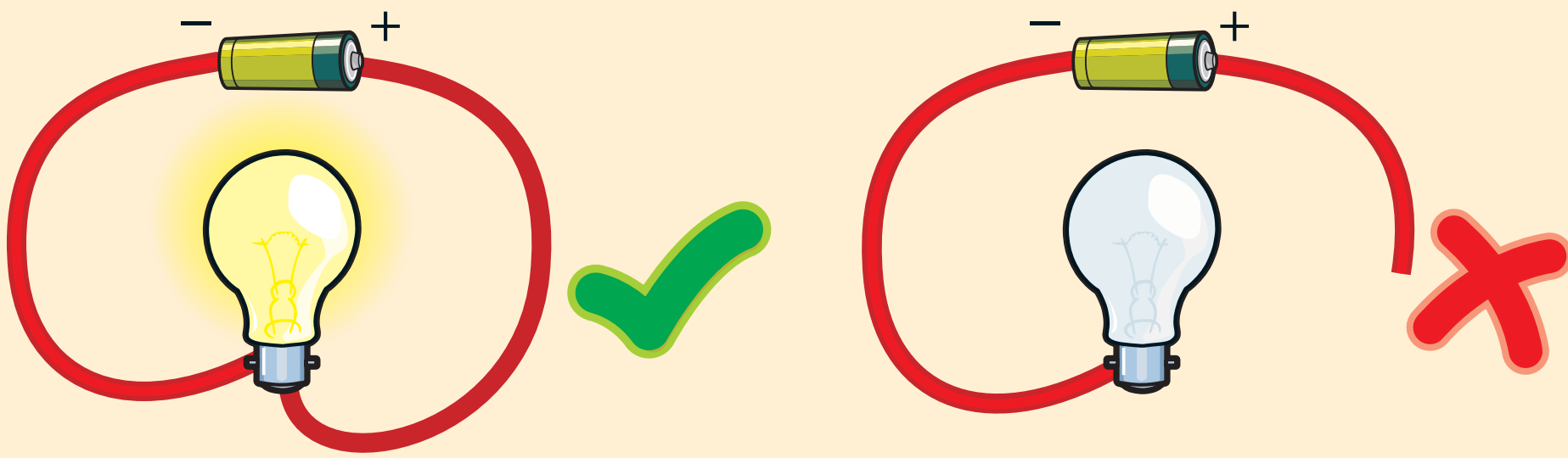


# ELECTRICAL CIRCUITS

Electric current is the flow of charge around a circuit.


## CIRCUIT

Electric current can only flow if there is a complete circuit. Any gaps will stop the current flowing.




- In a circuit, a battery provides the energy (voltage) to push charge around the circuit. A battery is made up of numerous connected cells.
- Ammeters are used to measure electric current.
- Current cannot be used up.

## CONVENTIONAL CURRENT



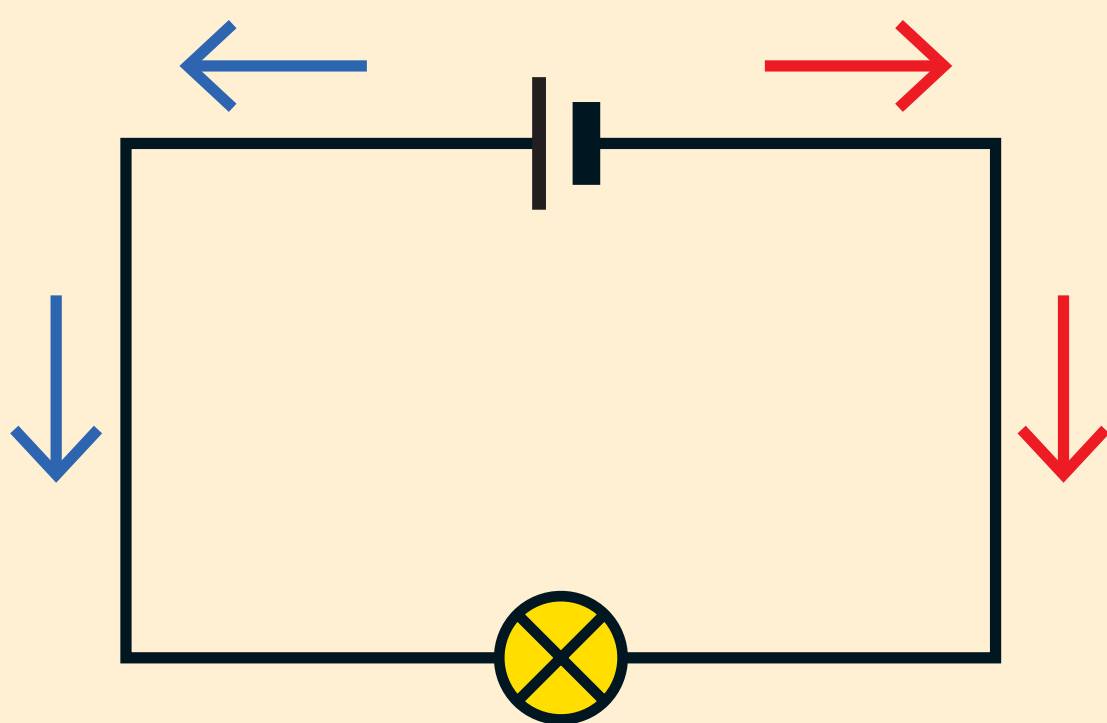


**Conventional current** is shown on circuits as flowing from positive to negative. However, the moving electrons actually have a **negative charge** and flow in the **opposite direction** to **conventional current**.

## SERIES CIRCUIT

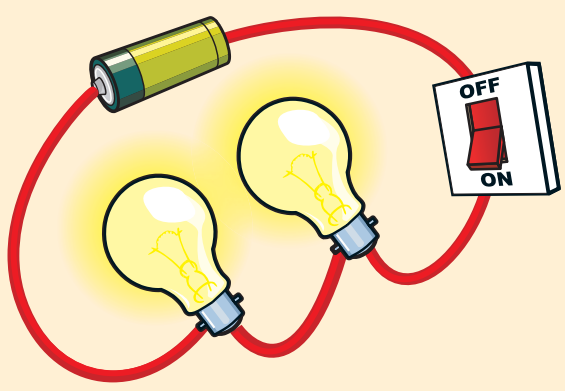


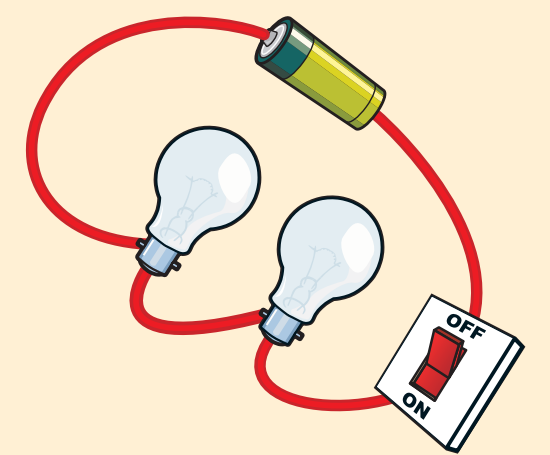
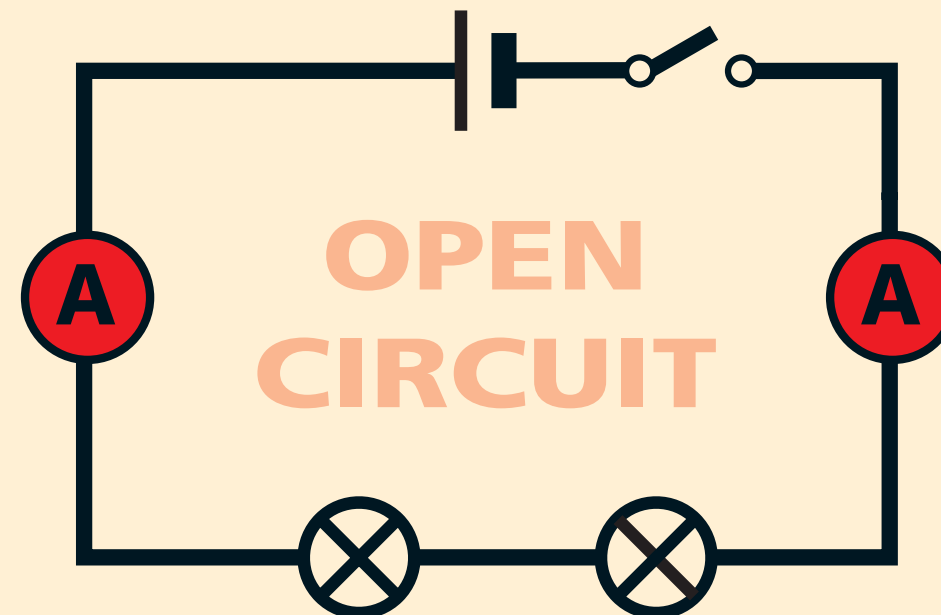
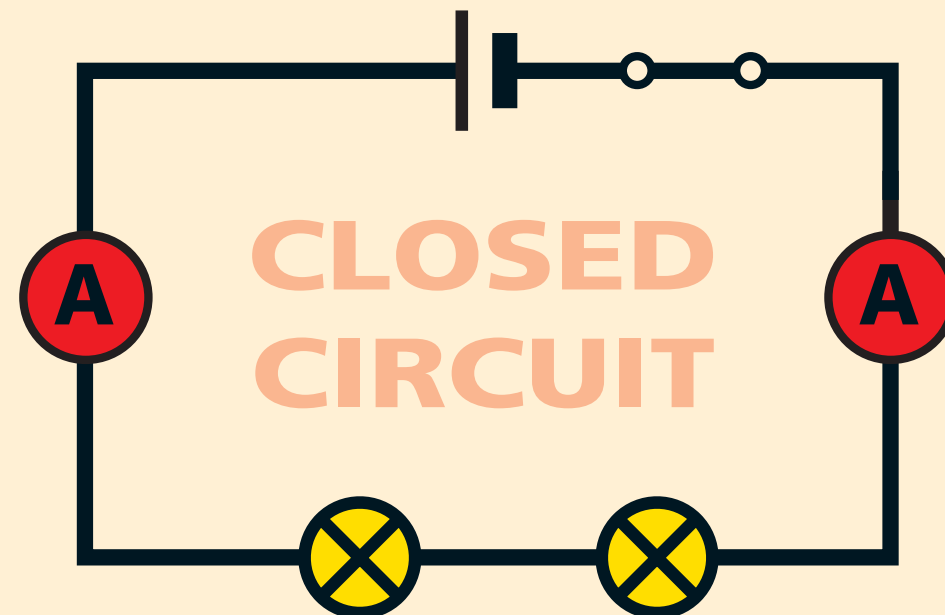
The electrics in computers, stereos and televisions contain series circuits.



- The current is the same anywhere in this circuit, as the current can only take one path.
- The current can be turned on (switch closed) or off (switch open).
- The more cells in the circuit, the brighter the bulbs will be.
- The more bulbs there are in the circuit, the more resistance against the current. Therefore, the bulbs will be dimmer.
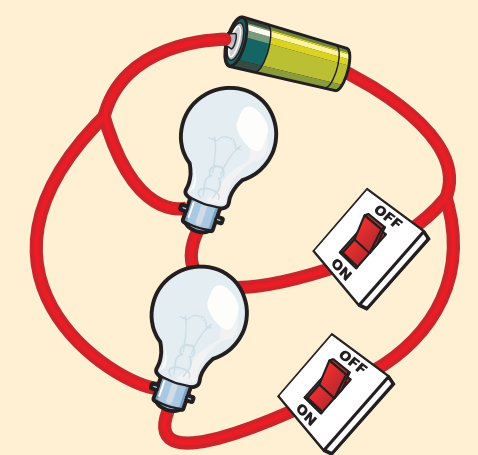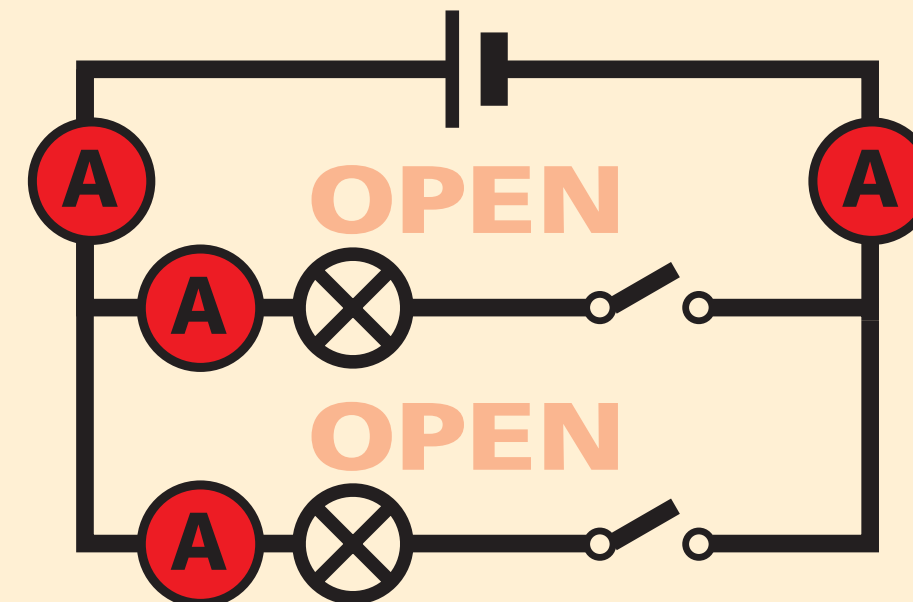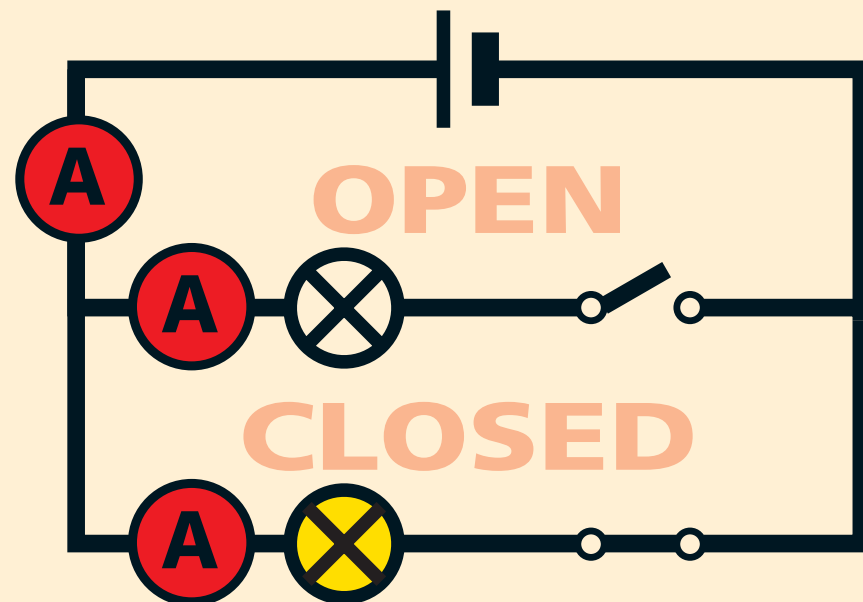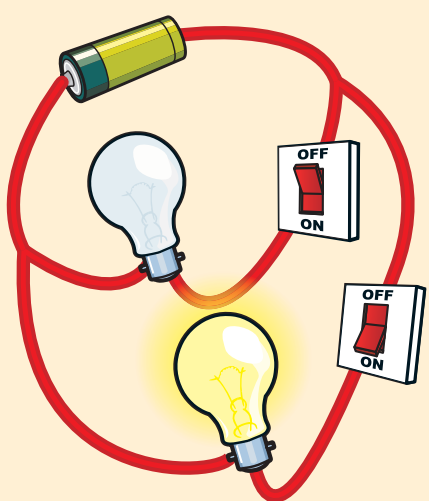
## PARALLEL CIRCUIT

The mains electricity in a house is a parallel circuit, allowing appliances to be used independently.



- The current takes more than one path.
- The current joins back up again on its way back to the battery. Therefore, the current is the same at the start and at the end of the circuit.
- Switches can be turned on or off to allow or restrict the flow to one or more parts of the circuit.
- **Remember:** Current is not used up.